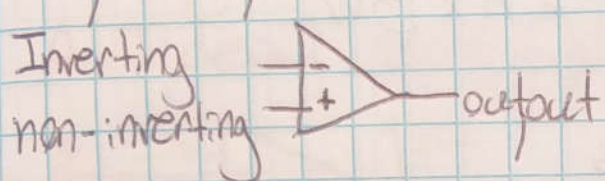


# Operational Amplifier (linear)


Acts in conjunction with outside feed back from other components

Feedback: resistance, capacitive

Op-Amp is a 3 terminal device



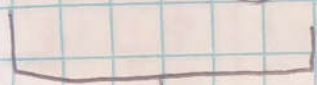output can sink or source either voltage or current



Input

4 types of gain

Voltage - volt

Current - curr

Transconductance - Volt

Transresistance - curr

most common


Voltage output =  $\beta(I_{nv} - nI_{nv})$

Diff amp

- a dual supply  $V_{cc}$  &  $V_{EE}$  ensures constant supply

- The voltage that appears at the output is the difference between the two ~~to~~ inputs

- inputs are antiphase

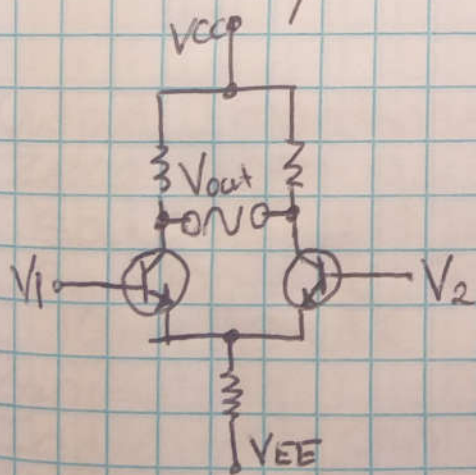

Inputs are identical

This is common mode of operation with common

mode gain being gain when input is zero

Real life there is some variation CM Rejection Ratio



$$\text{Voltage gain (A)} = \frac{V_{out}}{V_{in}}$$

$$\text{GBP} = \text{Gain} \times \text{Bandwidth} = A \times \text{BW}$$

Convert gain to decibels


$$20 \log(A) \text{ or } 20 \log \frac{V_{out}}{V_{in}}$$

an amplifiers band width  
is inversely proportional to gain



Op-amps naturally have very high gain when open loop  
 gain can be controlled by applying negative feedback

## An Ideal Op-Amp

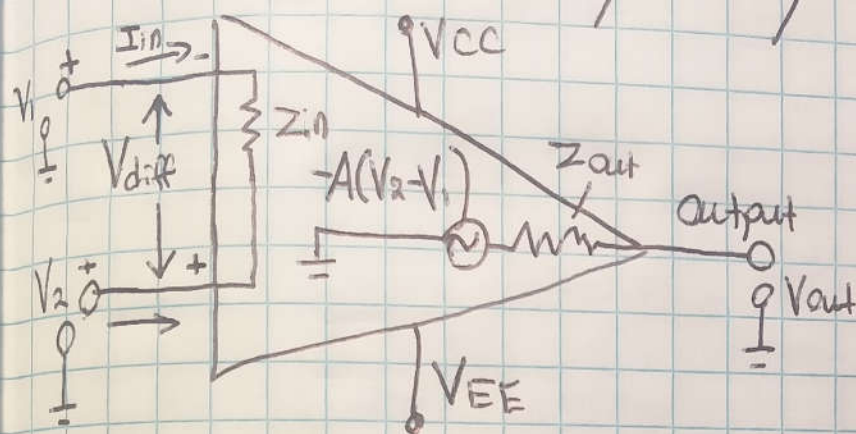

Open loop gain (A) (Infinite)  
 gain without feedback  
 (usually between 20,000 & 200,000) the higher the better

Input Impedance ( $Z_{in}$ )  
 Ideally Infinite

prevent supply current from leaking into input circuitry.

real amps between a few pico-amps & a few milli-amps

Output Impedance ( $Z_{out}$ )

Zero acts as a perfect Internal voltage source allowing the load to be fully supported. in reality is between  $100\Omega - 20k\Omega$

Bandwidth

Infinite An Ideal Amp has an infinite freq response. In real amps it is limited to ~~the place~~ the Gain Bandwidth product which is the freq where the amps gain becomes unity.

Offset Voltage ( $V_{io}$ )  
 Zero - The output should be zero when the Input difference is zero



# Inverting Op Amp


To reduce the substantial amount of gain the Amp must have feed back

Negative feed back is feeding a portion of the output to the negative or inverting input

To do this we use a feedback resistor this produces Closed-Loop Gain


What goes into the amp is a sum of both input & some output

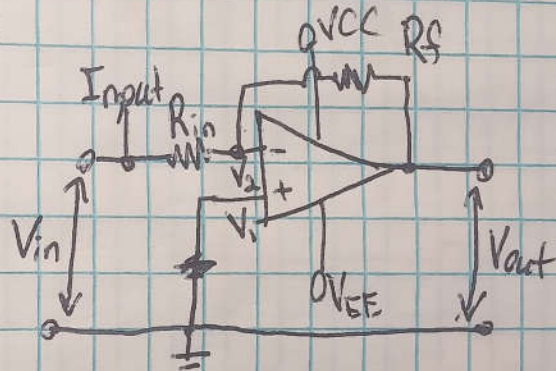The input needs to be separated from the inverting pin by a resistor to limit the current that can flow back into the input




Rules: no current flows into the inputs &  $V_a = V_i$  always
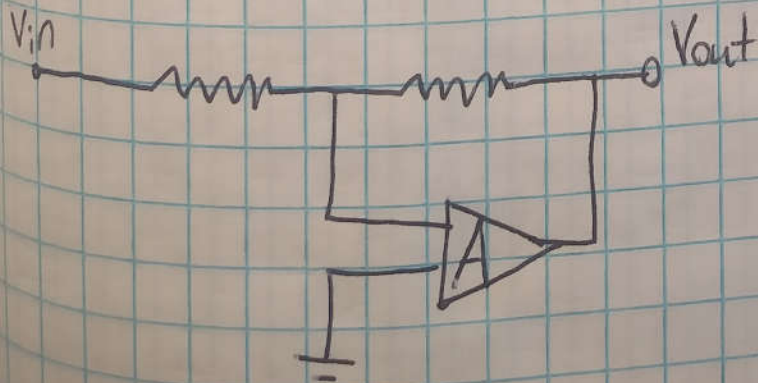
$$\text{Gain } (A_v) = \frac{V_{out}}{V_{in}} = -\frac{R_f}{R_{in}} \quad \text{or} \quad V_{out} = -\frac{R_f}{R_{in}} \cdot V_{in}$$





## Transresistance Amp


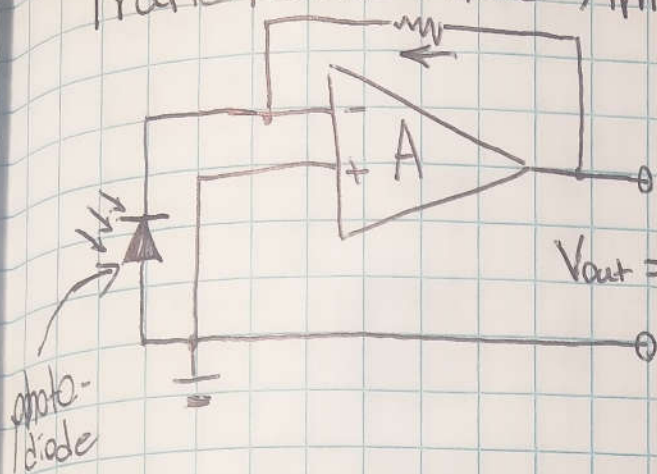


Converts a small current into a measurable voltage

$$V_{out} = -I_s \times R_f$$

Voltage output is proportional to the current generated

## Non-Inverting

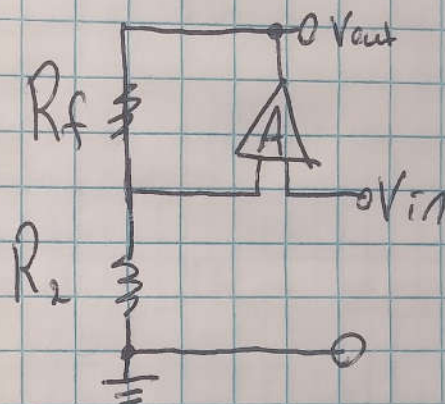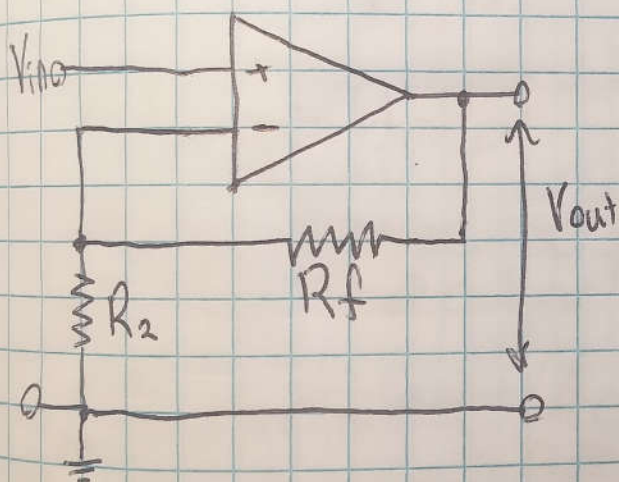


$$A = 1 + \frac{R_f}{R_2}$$

The gain will always be greater than one and if the  $R_f$  is zero then the gain will always be at unity (1) as  $R_2$  decreases the amplification increases towards infinity.

if  $R_2 = \text{infinity}$  &  $R_f = 0$  this produces a Voltage follower or Unity gain Buffer allows for circuit isolation and increasing available current without changing voltage.



# Unity Gain Buffer

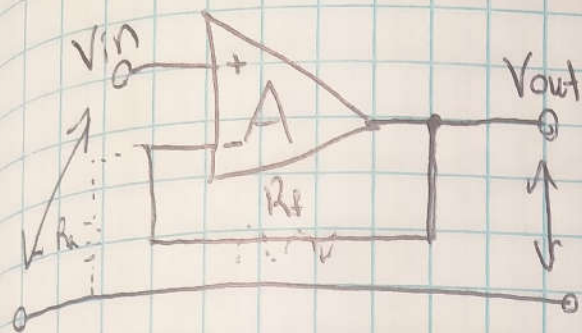

$$R_f = 0$$

$$R_2 = \text{infinity}$$


Can provide substantially more power at a consistent voltage

used to isolate circuits from each other especially in high-order state variable or active filters to separate filter stages (Sallen-Key type ~~buffer~~ filters)

requires zero current & thus zero voltage drop

often times a 1k resistor will be placed in the feed back loop to limit current

## Summing Amp

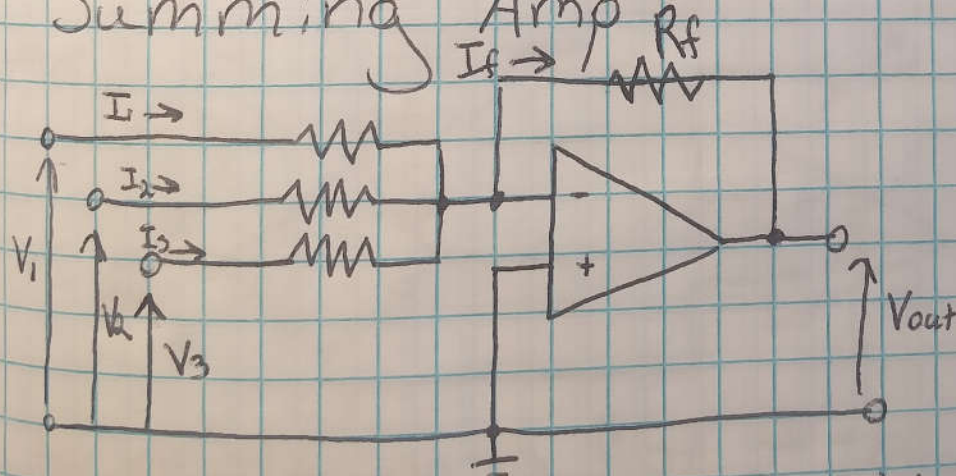


$$I_f = I_1 + I_2 + I_3$$

$$-V_{out} = \frac{V_1 R_f}{R_1} + \frac{V_2 R_f}{R_2} + \frac{V_3 R_f}{R_3}$$

applications as an audio mixer, digital to analog converter summing things and choosing their weight before summing



## Differential Amp

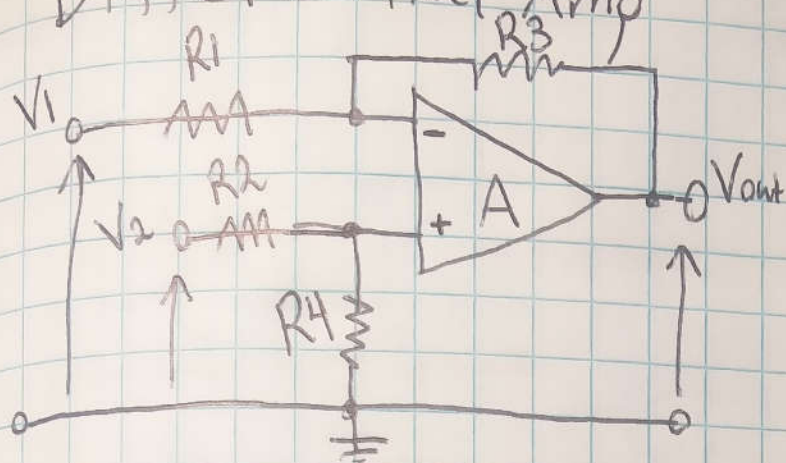

all amps are essentially differential amps as the output is proportional to the difference between inputs

$$V_{out} = -V_1 \left( \frac{R_3}{R_1} \right) + V_2 \left( \frac{R_4}{R_2 + R_4} \right) \left( \frac{R_1 + R_3}{R_1} \right)$$


When  $R_1 = R_2$  &  $R_3 = R_4$

$$V_{out} = \frac{R_3}{R_1} (V_2 - V_1)$$

If all resistors are equal the system becomes a unity gain diff amp and  $V_{out} = V_2 - V_1$

## Types of Diffamps

### Comparator

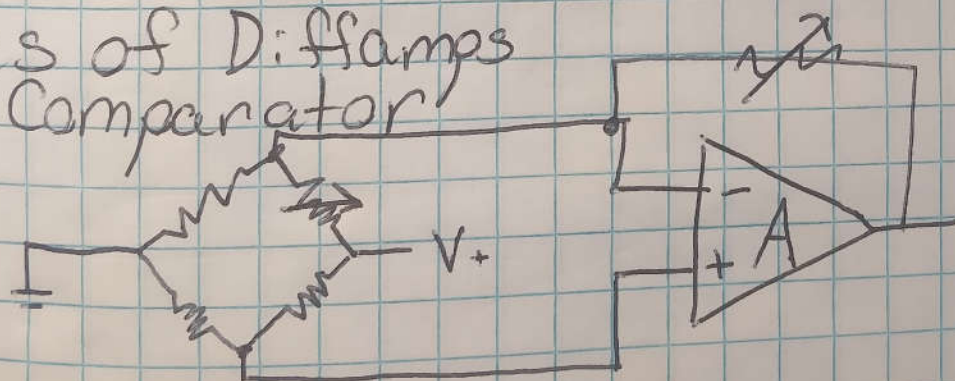


by replacing a foot of the bridge with some type of variable resistor like a thermistor or a Light dependent resistor the output can be as sensitive as the bridge + feedback allow



## High input impedance

## Instrumentation Amp

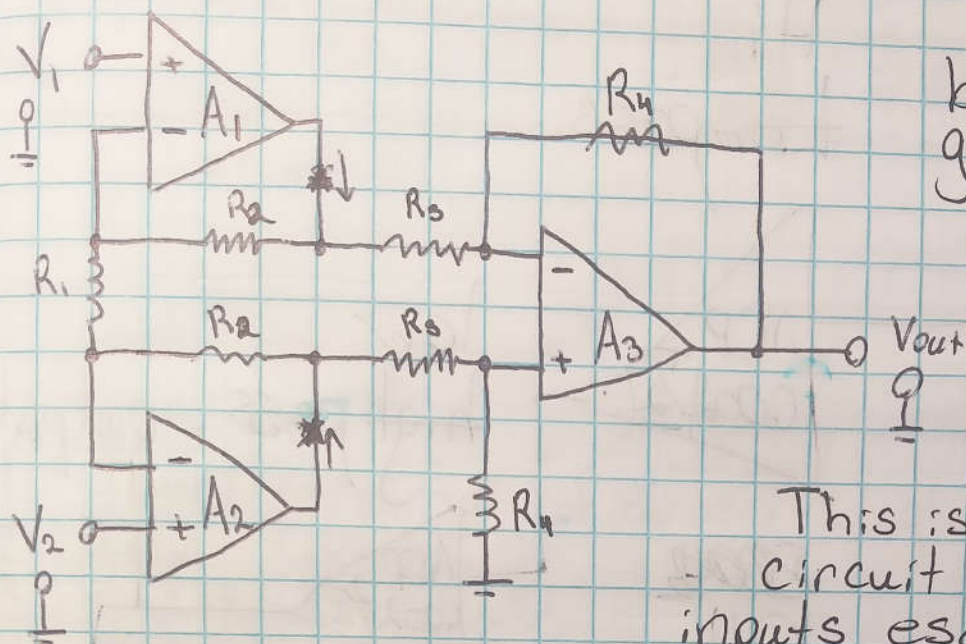


A1 & A2 act as buffers with a gain of

$$1 + \frac{2R_2}{R_1} = \beta(A)$$

$$V_{out} = (V_2 - V_1) \left[ 1 + \frac{2R_2}{R_1} \right] \left( \frac{R_4}{R_5} \right)$$

This isolates the circuit by making the inputs essentially infinitely higher impedance than the unity buffer amps


## The integrator Amp

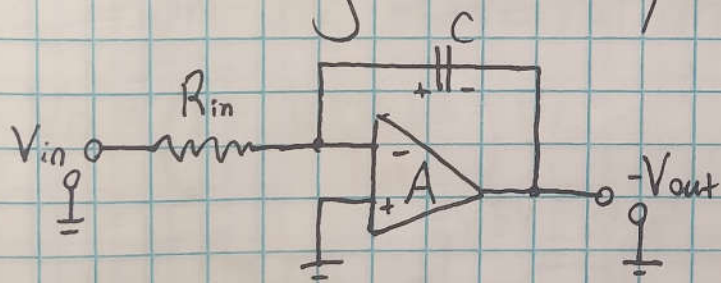

replaces the  $R_f$  of an inverting amp with a Cap



# Quick Oscilloscope Probe

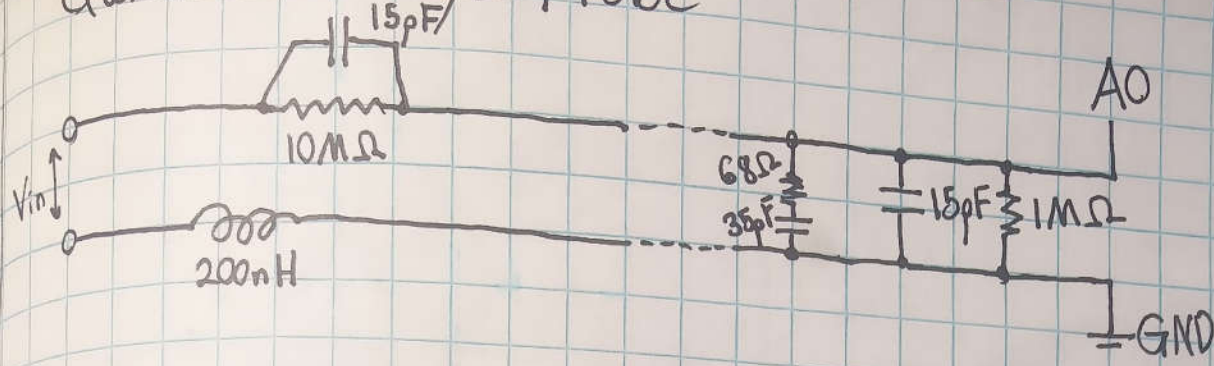


## AD623


- 1 Invert terminal of external gain setting resistor
- 2 Inv - Input (-)
- 3 n-Inv Input (+)
- 4  $V_{EE} -$
- 5 Ref input establishes common mod voltage
- 6 Output +
- 7  $V_{CC} +$
- 8 non-inv external gain setting

$$V_o = \left(1 + \frac{100k\Omega}{R_G}\right) V_c$$

Signal  $a_q$

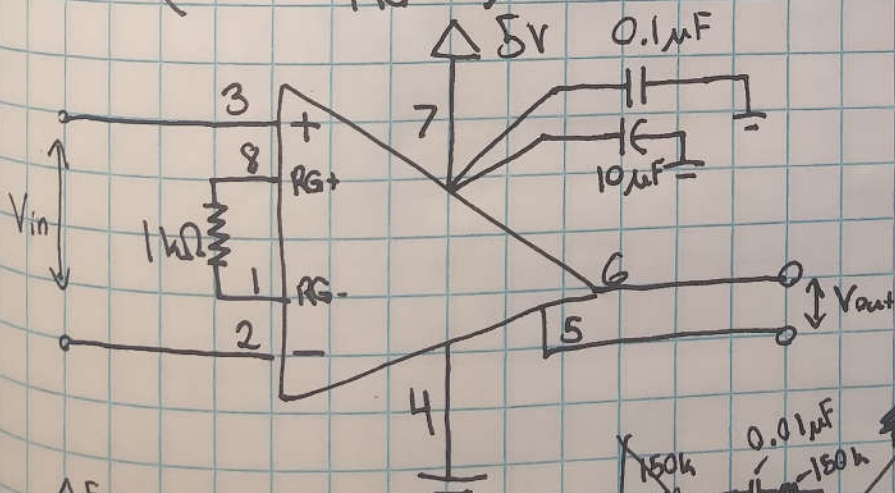



Gain = ~ 100

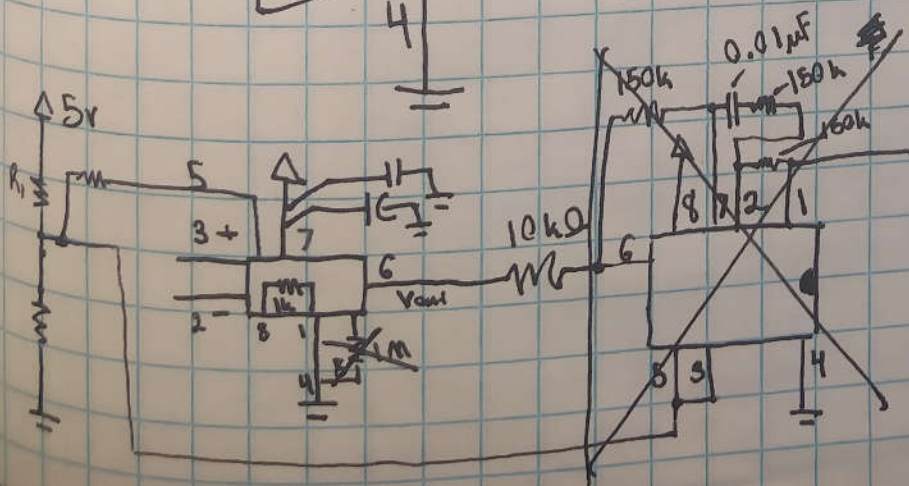



# Board Diagram


Jumper

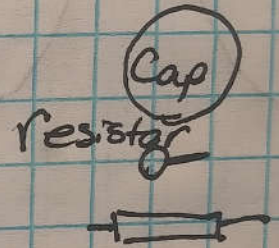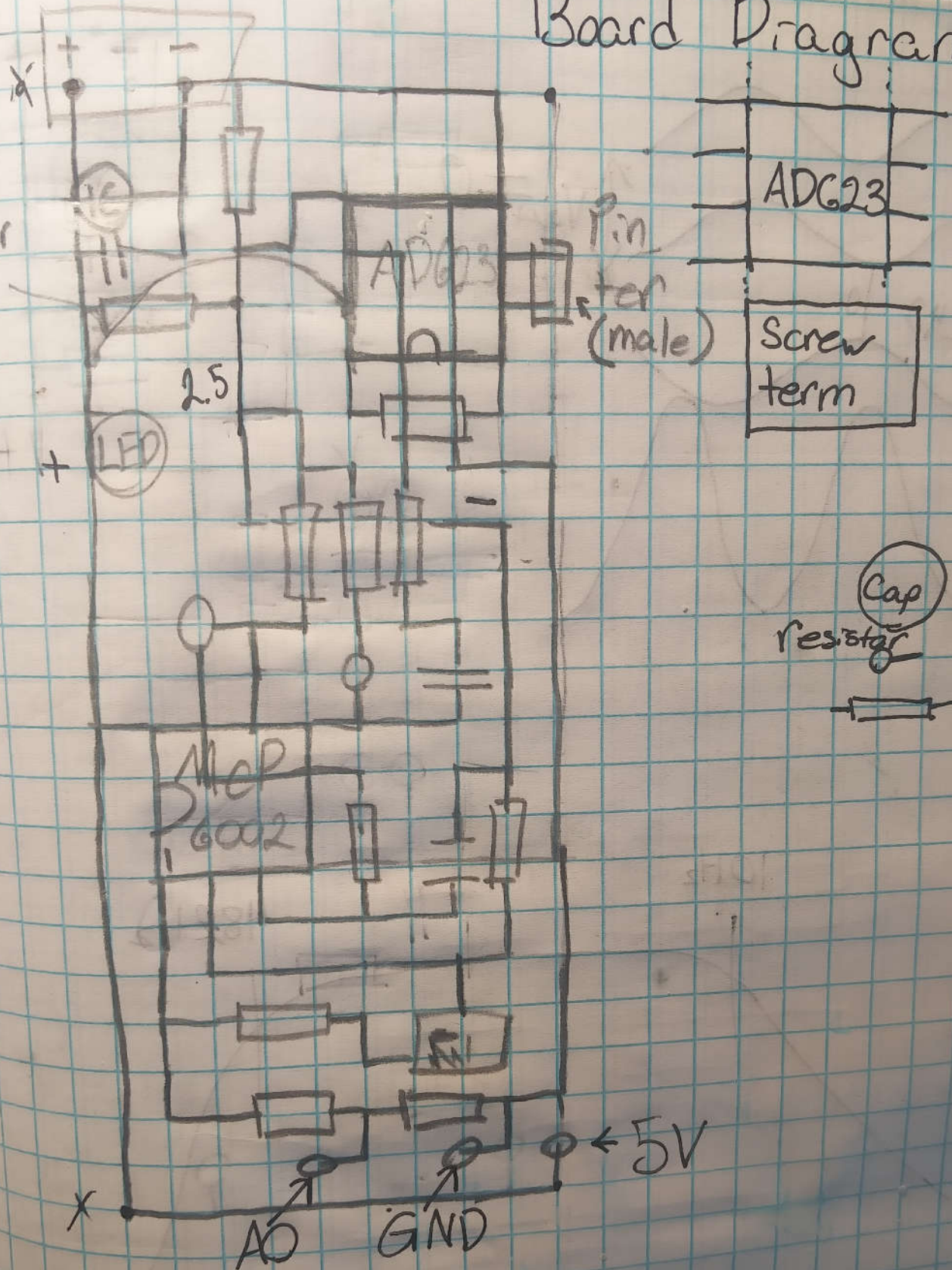




# low pass filter

MCP6002(1/2)

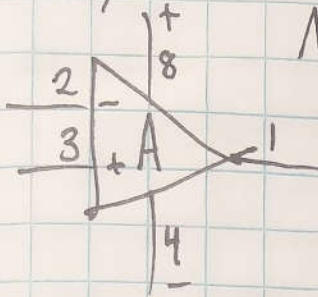

Highpass  
from Inverting Amp

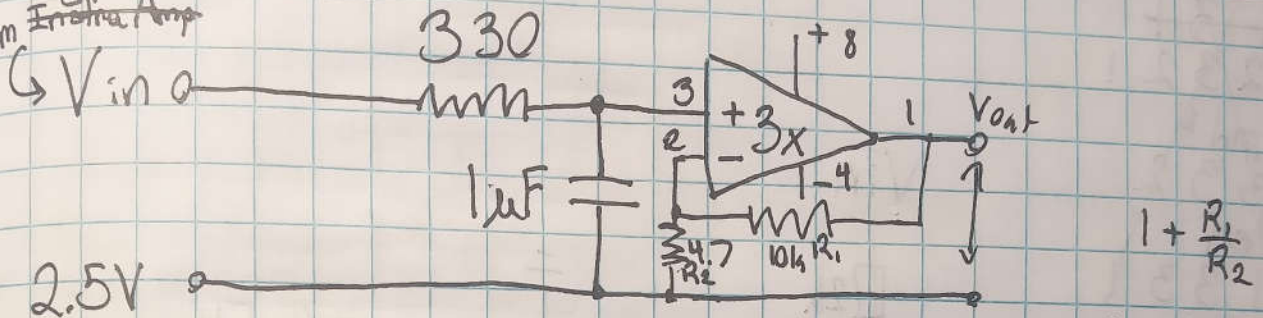

$$f_c \approx 500 \text{ Hz}$$


$$\frac{1}{2\pi(330)(1 \times 10^{-6})} = \boxed{482 \text{ Hz}}$$

$$3.128 = 1 + \left(\frac{10k}{4.7k}\right) = A$$
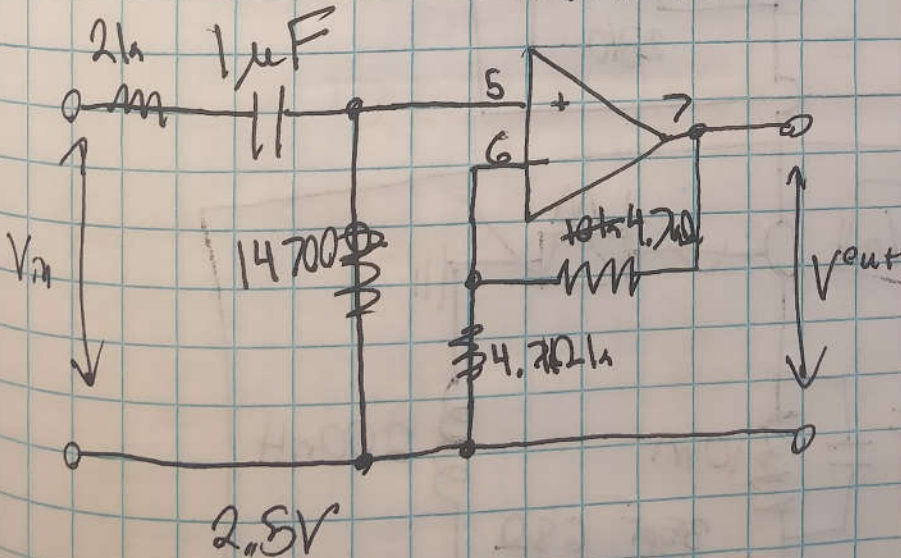
# Highpass filter

$$f_c \approx 10 \text{ Hz}$$

$$\frac{1}{2\pi(1 \times 10^{-6})(14700)} = \boxed{10.83 \text{ Hz}}$$



$$\frac{10k}{4.7}$$